

# Wiring Diagram for Arduino Controlled Bot

## Wiring Diagram Instructions:

### 1. L298N Motor Driver Connections:

- Motor 1 (Left Motor):
  - OUT1 -> Left Motor +, OUT2 -> Left Motor -
- Motor 2 (Right Motor):
  - OUT3 -> Right Motor +, OUT4 -> Right Motor -
- EN1 to Pin 9 on Arduino (Motor 1 PWM)
- EN2 to Pin 10 on Arduino (Motor 2 PWM)
- IN1 to Pin 7 on Arduino (Motor 1 Direction Control)
- IN2 to Pin 6 on Arduino (Motor 1 Direction Control)
- IN3 to Pin 5 on Arduino (Motor 2 Direction Control)
- IN4 to Pin 4 on Arduino (Motor 2 Direction Control)
- +12V Power Input to + Terminal of 3S LiPo Battery
- GND on L298N to - Terminal of 3S LiPo Battery

### 2. Arduino Power:

- Connect the 5V output from the L298N to the 5V pin on Arduino, or use a dedicated 5V regulator.

### 3. HC-05 Bluetooth Module:

- VCC to 5V on Arduino
- GND to GND on Arduino
- RXD to TX on Arduino (with level shifter if needed)
- TXD to RX on Arduino

#### 4. Additional Notes:

- Ensure a common ground connection among all components.
- Securely mount the 3S LiPo battery with heat-resistant insulation if possible.